

ELECTRIC CIRCUITS

Seventh Edition

DAVID A. BELL

*Lambton College of Applied Arts and Technology
Sarnia, Ontario, Canada*

OXFORD
UNIVERSITY PRESS

OXFORD
UNIVERSITY PRESS

YMCA Library Building, Jai Singh Road, New Delhi 110001

Oxford University Press is a department of the University of Oxford.
It furthers the University's objective of excellence in research, scholarship,
and education by publishing worldwide in

Oxford New York
Auckland Cape Town Dar es Salaam Hong Kong Karachi
Kuala Lumpur Madrid Melbourne Mexico City Nairobi
New Delhi Shanghai Taipei Toronto

With offices in
Argentina Austria Brazil Chile Czech Republic France Greece
Guatemala Hungary Italy Japan Poland Portugal Singapore
South Korea Switzerland Thailand Turkey Ukraine Vietnam

Oxford is a registered trade mark of Oxford University Press
in the UK and in certain other countries.

Original seventh edition published by and © Oxford University Press,
70 Wynford Drive, Don Mills, Ontario, Canada.

Previous editions published by Prentice-Hall, Inc.

This adapted edition first published in 2009
by Oxford University Press India

© Oxford University Press 2009

The moral rights of the author/s have been asserted.

Database right Oxford University Press (maker)

All rights reserved. No part of this publication may be reproduced,
stored in a retrieval system, or transmitted, in any form or by any means,
without the prior permission in writing of Oxford University Press,
or as expressly permitted by law, or under terms agreed with the appropriate
reprographics rights organization. Enquiries concerning reproduction
outside the scope of the above should be sent to the Rights Department,
Oxford University Press, at the address above.

You must not circulate this book in any other binding or cover
and you must impose this same condition on any acquirer.

ISBN-13: 978-0-19-569428-4
ISBN-10: 0-19-569428-7

Typeset in Palatino Roman
by Archetype, New Delhi 110063
Printed in India by Ram Book Binding House, New Delhi 110020
and published by Oxford University Press
YMCA Library Building, Jai Singh Road, New Delhi 110001

CONTENTS

Preface	iii
Important Equations	xx
Chapter 1 Basics of Electricity	1
1-1 Electrification by Friction	2
1-2 Voltage, Current, and Resistance	4
1-3 Basic Source of Electricity	5
1-4 Electric Lamp	7
1-5 Electric Circuit	8
1-6 Current Direction	9
1-7 Direct Current and Alternating Current	10
1-8 Electric Shock	10
Chapter 2 Measuring Current, Voltage, and Resistance	14
2-1 Metric Prefixes and Engineering Notation	14
Scientific Notation	14
Metric Prefixes	15
Engineering Notation	15
Significant Figures	16
2-2 Current Measurement	17
Unit of Current	17
Ammeter	17
Ammeter Connection	18
Digital Ammeter	18
Analog Ammeter	20
2-3 Voltage Measurement	22
Unit of Voltage	22
Voltmeter	22
Voltmeter Connection	22
Digital Voltmeter	22
Analog Voltmeter	23
2-4 Resistance Measurement	24
Unit of Resistance	24
Ohmmeter	24
Digital Ohmmeter	25
Analog Ohmmeter	25
2-5 Instrument Accuracy and Precision	27
Digital Instrument Accuracy	27
Analog Instrument Accuracy	27
Precision	28
Chapter 3 Ohm's Law and Electrical Calculations	34
3-1 Resistance	34
3-2 Ohm's Law	36

3-3	Application of Ohm's Law	38
3-4	Conductance	41
3-5	Electrical Power and Energy	42
	Power Dissipation	42
	Efficiency	45
	Electrical Energy	46
Chapter 4	Conductors, Insulators, and Resistors	52
4-1	Conductors	53
	Conducting Materials	53
	Conductor Calculations	53
4-2	Insulators	57
	Insulating Materials	57
	Insulator Calculations	58
4-3	Conductor Resistivity	60
4-4	Temperature Effects on Conductors	64
4-5	Resistor Construction and Power Rating	69
	Fixed-value Resistors	69
	Variable Resistors	69
	Resistor Tolerance	70
	Resistor Networks	71
	Photoconductive Cell	71
	Low-Power Variable Resistor	72
	High-Power Resistor	72
	Resistor Power Ratings	72
4-6	Temperature Coefficient of Resistors	74
4-7	Resistor Color Code	76
Chapter 5	Series Resistor Circuits	83
5-1	Series Resistor Circuit	83
	Series-Connected Resistors	83
	Equivalent Resistance	85
	Current Levels	85
5-2	Voltages in a Series Circuit (Kirchhoff's Voltage Law)	87
	Resistor Voltage Drops	87
	Kirchhoff's Voltage Law	88
	Circuit Ground	88
	Series-Connected Voltage Sources	89
5-3	Voltage Divider	92
	Circuit and Equations	92
	Voltage-Divider Theorem	93
	Voltage-Divider Design	95
5-4	Potentiometer	96
5-5	Power in a Series Circuit	99
5-6	Voltage Dropping and Current Limiting	101
5-7	Open-Circuits and Short-Circuits in Series Circuits	103

Chapter 6	Parallel Resistor Circuits	112
6-1	Parallel Resistor Circuit (Kirchhoff's Current Law) Parallel-Connected Resistors 113 Current Levels 113 Kirchhoff's Current Law 114	113
6-2	Parallel Equivalent Circuit Equivalent Resistance 117	117
6-3	Conductances in Parallel	120
6-4	Current Divider	122
6-5	Power in Parallel Circuits	127
6-6	Open-Circuits and Short-Circuits in Parallel Circuits	129
Chapter 7	Series-Parallel Resistor Circuits	136
7-1	Series-Parallel Resistor Circuits Simple Series-Parallel Circuit 136 Series-Parallel Equivalent Circuits 137	136
7-2	Currents in a Series-Parallel Circuit	139
7-3	Voltage Drops in a Series-Parallel Circuit	141
7-4	Ladder Networks	144
7-5	Analysis of Series-Parallel Resistor Circuits	147
7-6	Trouble-Shooting Series-Parallel Circuits Open-Circuits and Short-Circuits 151 Trouble-Shooting 154	151
Chapter 8	Network Analysis Techniques	159
8-1	Voltage Sources and Current Sources Voltage Source 159 Current Source 160 Source Conversions 161 Parallel and Series Operation 164	159
8-2	Dependent Voltage and Current sources Externally Dependent Sources 166 Circuit Dependent Sources 167	166
8-3	Network Analysis Using Kirchhoff's Laws Use of Determinants 171	168
8-4	Loop (Mesh) Equations	174
8-5	Nodal Analysis	178
8-6	Δ -Y Transformations	184
Chapter 9	Network Theorems	196
9-1	The Superposition Theorem	197
9-2	Thévenin's Theorem	201
9-3	Norton's Theorem	206
9-4	Millman's Theorem	209
9-5	Maximum Power Transfer Theorem	212
9-6	Reciprocity theorem	213
9-7	Compensation Theorem	216
9-8	Tellegen's Theorem	218

Chapter 10	Voltage Cells, Batteries, and DC Power Supplies	226
10-1	Simple Voltage Cell	227
10-2	Voltage Cell Characteristics	228
	Polarization 228	
	Output Voltage and Current 228	
	Ampere-Hour Rating 228	
	Primary and Secondary Cells 230	
	Cell Equivalent Circuit 231	
10-3	Miscellaneous Voltage Cells	233
	Zinc-Carbon Cell 233	
	Manganese-Alkaline Cell 235	
	Mercury Cell 235	
	Comparison of Primary Cells 235	
	Rechargeable Cells 235	
	Solar Cell 236	
10-4	Voltage Cells in Series	237
	Output Voltage and Current 237	
	9 V Battery 239	
	Series-Aiding and Series-Opposing 240	
	Plus/Minus Supply 241	
10-5	Voltage Cells in Parallel	242
10-6	Voltage Cells in Series-Parallel	245
10-7	Lead-Acid Battery	247
	Construction 247	
	Operation 248	
	Ampere-Hour Rating of Lead-Acid Battery 249	
	Charging 251	
	Specific Gravity 252	
	Care of Lead-Acid Batteries 252	
10-8	DC Power Supplies	253
	Laboratory Power Supplies 253	
	Portable DC Power Supplies 254	
Chapter 11	Magnetism	261
11-1	Magnetic Field	262
	North and South Poles 262	
	Magnetic Lines of Force 262	
11-2	Electromagnetism	266
	Magnetic Field Around a Conductor 266	
	Magnetic Field Around a Coil 269	
	Electromagnetic Induction 270	
11-3	Theory of Magnetism	272
11-4	Magnetic Flux and Flux Density	273
11-5	Magnetomotive Force and Magnetic Field Strength	275
11-6	Force on Current-Carrying Conductors	277
	Force on a Conductor 277	
	Force on a Coil 279	
	PMMC Instruments 281	

Chapter 12	Magnetic Circuits	288
12-1	Reluctance and Permeability	289
12-2	Permeability of Free Space	291
12-3	Solenoid	294
12-4	Relative Permeability	295
12-5	Composite Magnetic Circuits	299
12-6	Force between Two Magnetic Surfaces	303
12-7	Magnetization Curves, Hysteresis, and Eddy Currents	306
	Magnetization Curves	306
	Hysteresis	309
	Eddy Currents	311
Chapter 13	DC Measuring Instruments	318
13-1	Basic Ammeters	319
	Analog DC Ammeter Circuit	319
	Ammeter Resistance	320
	Multirange Ammeters	321
	Ayrton Shunt	322
13-2	Basic Voltmeters	323
	Analog DC Voltmeter Circuit	323
	Multirange Voltmeters	323
	Voltmeter Resistance	325
13-3	Basic Ohmmeters	327
	Simple Ohmmeter Circuit	327
	Ohmmeter with Zero Adjust	329
13-4	Electronic Voltmeters (Analog and Digital)	330
	Analog Electronic Voltmeter	330
	Digital Voltmeter	333
13-5	Electronic Ammeters and Ohmmeters	335
	Electronic Ammeter	335
	Electronic Ohmmeter	336
13-6	Measuring Resistance by Ammeter and Voltmeter	338
13-7	The Megohmmeter	340
13-8	Power Measurement	341
13-9	The Wheatstone Bridge	343
Chapter 14	Inductance	351
14-1	Electromagnetic Induction	352
14-2	Induced EMF and Current	354
14-3	Self-Inductance	357
	Coil and Conductor Inductance	357
	Calculation of Self-Inductance	360
	Incremental Inductance	364
	Noninductive Coil	365
14-4	Mutual Inductance	366
14-5	Types of Inductors	370
	Power Supply Inductor	370

High-Frequency Inductor	371	
Molded Inductors	372	
Laboratory Inductors	372	
Stray Inductance	372	
14-6 Energy Stored in an Inductive Circuit		372
14-7 Inductors in Series and in Parallel		374
Series-Connected Inductors	374	
Parallel-Connected Inductors	375	
Inductors with Mutual Inductance	376	
Chapter 15	Capacitance	385
15-1 Electric Charge Storage		385
15-2 Electric Field		388
Electric Lines of Force	388	
Electric Charge, Flux, and Flux Density	389	
Dielectric Effects	389	
15-3 Capacitance and Capacitor Dimensions		392
Plate Area and Dielectric Thickness	392	
Permittivity	394	
Capacitance Equation	395	
15-4 Capacitor Types and Characteristics		398
Working Voltage	398	
Capacitor Tolerance	398	
Temperature Effects	398	
Leakage Current	399	
Capacitor Equivalent Circuit	399	
Air Capacitors	400	
Paper Capacitors	400	
Plastic Film Capacitors	400	
Mica Capacitors	401	
Ceramic Capacitors	401	
Electrolytic Capacitors	401	
Polarization	402	
Tantalum Capacitors	403	
Stray Capacitance	404	
Capacitor Identification Codes	404	
15-5 Capacitors in Series and in Parallel		405
Parallel-Connected Capacitors	405	
Series-Connected Capacitors	406	
15-6 Energy Stored in a Charged Capacitor		409
Chapter 16	Inductance and Capacitance in DC Circuits	416
16-1 <i>RL</i> Circuit Operation		417
16-2 Instantaneous Current and Voltage in <i>RL</i> Circuits (Step Response)		420
Current Equation	420	
Time Constant	421	
Counter-emf	422	

16-3	Open-Circuiting an Inductive Circuit (Source-Free Response)	424
	Counter-emf	424
	Controlling the Counter-emf	425
	Source-Free Response	427
16-4	<i>RL</i> Circuit Waveforms	428
16-5	<i>RC</i> Circuit Operation	429
16-6	Instantaneous Current and Voltage in <i>RC</i> Circuits (Step Response)	431
	Voltage Equation	431
	Time Constant	434
	Charging Current	434
16-7	Discharging a Capacitor (Source-Free Response)	436
	Capacitor Voltage	436
	Safe Discharging	437
	Source-Free Response	439
16-8	<i>RC</i> Circuit Waveforms	439
16-9	<i>RLC</i> Series Circuit	441
	Step Response	441
	Source-Free Response	444
Chapter 17 Alternating Current and Voltage		452
17-1	Generation of Alternating Voltage	453
17-2	Sine Wave	456
	Sinusoidal Waveform	456
	Instantaneous Voltage	458
17-3	Frequency, Phase Angle, and Wavelength	461
	Frequency	461
	Phase Angle	462
	Phase Difference	464
	Wavelength	465
17-4	Resistive Load with AC Supply	467
	Current Level	467
	Power Dissipation	468
17-5	Peak, Average, and RMS Values of Sine Waves	470
	Peak and Peak-to-Peak Values	470
	Average Value	470
	RMS Value	472
17-6	Oscilloscopes	476
	Basic Oscilloscope	476
	Oscilloscope Probes	476
	Oscilloscope Controls	477
	Measuring Voltage and Time Period	480
	Phase Difference Measurement	481
17-7	AC Function Generator	482
17-8	Basic AC Voltmeters	483
	PMMC Instrument on AC	483
	Rectification	484
	Rectifier Voltmeter	486

17-9	AC Electronic Voltmeters Voltmeter Circuit 488 Frequency Response of AC Electronic Instruments 489	488
Chapter 18	Phasors and Complex Numbers	496
18-1	Phasor Representation of Alternating Voltage Scalars and Vectors 496 Phasors 497	496
18-2	Addition and Subtraction of Phasors Phasor Addition 498 Phasor Subtraction 502	498
18-3	Polar and Rectangular Forms, the j Operator Polar Form 504 Rectangular Form, the j Operator 505	504
18-4	Mathematics of Complex Quantities Addition and Subtraction 508 Multiplication 508 Division 509 Polar Form Mathematics 510	508
Chapter 19	Inductance and Capacitance in AC Circuits	514
19-1	Alternating Current and Voltage in an Inductive Circuit	515
19-2	Inductive Reactance and Susceptance Inductive Reactance 517 Inductive Susceptance 519 Effect of Mutual Inductance 521	517
19-3	Alternating Current and Voltage in a Capacitive Circuit	522
19-4	Capacitive Reactance and Susceptance Capacitive Reactance 523 Capacitive Susceptance 524	523
19-5	Series RL Circuits Current and Voltage Waveforms 526 Phasor Diagram 527 Circuit Equations 527 Impedance Diagram 528 Admittance 529 Practical Inductors 529	526
19-6	Series RC Circuits Current and Voltage Waveforms 533 Phasor Diagram 534 Circuit Equations 534 Impedance Diagram 535 Locus Diagram 537	533
19-7	Series RLC Circuits Circuit 539 Phasor Diagram 540 Circuit Equations 540	539

Impedance Diagrams	541	
19-8 Parallel <i>RL</i> Circuits		544
Circuit and Phasor Diagrams	544	
Circuit Equations	544	
Admittance Diagram	545	
19-9 Parallel <i>RC</i> Circuits		547
Circuit and Phasor Diagrams	547	
Circuit Equations	547	
Admittance Diagram	548	
19-10 Parallel <i>RLC</i> Circuits		549
Phasor Diagrams	549	
Circuit Equations	550	
Admittance Diagram	551	
Chapter 20	Series and Parallel AC Circuits	562
20-1 Series-Connected Impedances		563
20-2 AC Voltage Divider		565
Multi-Component Voltage Divider	565	
Compensated Oscilloscope Probe	566	
20-3 Impedances in Parallel		568
20-4 AC Current Divider		573
20-5 Series-Parallel Impedances		576
20-6 Series and Parallel Equivalent Circuits		579
Chapter 21	Power in AC Circuits	587
21-1 Power Dissipated in a Resistance		588
21-2 Power in an Inductance		589
21-3 Power in a Capacitance		592
21-4 True Power and Reactive Power		594
21-5 Power in <i>RL</i> and <i>RC</i> Circuits		596
<i>RL</i> Circuit Power	596	
<i>RC</i> Circuit Power	598	
21-6 Power Factor		602
Power Factor Equation and Power Triangle	602	
Power Factor Correction	603	
21-7 AC Wattmeter		607
Chapter 22	AC Network Analysis and Theorems	615
22-1 AC Voltage and Current Sources		616
AC Sources	616	
AC Source Conversion	617	
22-2 Kirchhoff's Laws for AC Circuits		619
22-3 AC Circuit Loop Equations (Mesh Equations)		622
Circuit with Independent Sources	623	
Circuit with a Dependent Source	625	
22-4 Superposition Theorem Applied to AC Networks		628
22-5 Nodal Analysis for AC Circuits		630

	Circuit with Independent Sources	631
	Circuit with a Dependent Source	633
22-6	Thévenin's Theorem Applied to AC Circuits	635
22-7	Norton's Theorem Applied to AC Circuits	638
22-8	Maximum Power Transfer Theorem Applied to AC Circuits	640
22-9	Reciprocity Theorem Applied to AC Circuits	643
22-10	Compensation Theorem Applied to AC Circuits	646
22-11	Δ -Y Transformations for AC Networks	647
22-12	AC Bridges	650
	Simple Capacitance Bridge	650
	Series-Resistance Capacitance Bridge	651
	Inductance Bridges	653
Chapter 23	Resonance	666
23-1	Series Resonance	667
	Frequency Effect on Circuit Impedance	667
	Current at Resonance	669
	Phase Angle	669
	Resonance Frequency	669
	Resonance Rise in Voltage	672
	Energy Transfer between L and C	675
23-2	Tuning for Resonance	675
23-3	Q Factor of a Series Resonant Circuit	677
23-4	Bandwidth of a Series Resonant Circuit	679
23-5	Parallel Resonance	683
	Ideal Parallel Resonant Circuit	683
	Practical Parallel Resonant Circuit	684
	Phase Angle	686
23-6	Q Factor for Parallel LC Circuits	688
23-7	Resonance Frequency for Parallel LC Circuits	689
23-8	Resistance Damping of Parallel LC Circuits	692
23-9	Tuned Coupled Coils	694
	Coupled Coils	694
	Coupled Impedance	695
	Coefficient of Coupling	697
Chapter 24	Filters	709
24-1	Basic Filter Types	710
24-2	Power Measurement in Decibels	711
24-3	RC Low-Pass Filters	713
	RC Low-Pass Filter Circuit	713
	Gain/Frequency Response	714
	Insertion Loss	716
	Phase/Frequency Response	716
	Low-Pass Filter Transfer Function	718
24-4	RC High-Pass Filters	720
	RC High-Pass Filter Circuit	720
	Frequency Response Graphs	720

Insertion Loss	722
High-Pass Filter Transfer Function	722
24-5 Filter Frequency Response Graphs	724
Low-Pass Straight-Line Approximations	724
Drawing the Actual Low-Pass Frequency Response Graphs	726
Selecting f_c on the Frequency Response Graphs	728
High-Pass Straight-Line Approximations	729
Drawing the Actual High-Pass Frequency Response Graphs	731
24-6 RL Low-Pass and High-Pass Filters	732
RL Low-Pass Filter	732
RL High-Pass Filter	733
24-7 Bandpass Filters	735
High-Pass Low-Pass Combination for Bandpass	735
Series Resonant Bandpass Filter	736
Parallel Resonant Bandpass Filter	739
24-8 Notch Filters	741
High-Pass Low-Pass Combination for Notch	741
Notch Filters Using Resonant Circuits	742
Chapter 25 Transformers	752
25-1 Principle of Transformer Operation	753
Transformer Construction	753
Primary and Secondary Voltages	754
Step-Up, Step-Down and Multi-Output Transformers	754
Primary and Secondary Currents	757
25-2 EMF Equation	760
25-3 Transformer on No-Load	761
Core Losses	761
No-Load Phasor Diagram	762
No-Load Equivalent Circuit	763
25-4 Transformer on Load	764
Leakage Inductance	764
Complete Equivalent Circuit	764
Phasor Diagram for Secondary	765
Phasor Diagram for Primary	767
25-5 Referred Resistance and Reactance	769
Referred Quantities	769
Simplification of Equivalent Circuit	770
25-6 Transformer Voltage Regulation	773
25-7 Transformer Efficiency	775
25-8 Open-Circuit and Short-Circuit Tests	778
Open-Circuit Test	778
Short-Circuit Test	780
25-9 Autotransformer, Current Transformer, and Audio Transformer	783
Autotransformer	783
Current Transformer	784
Audio Transformer	786

Chapter 26	Three-Phase AC Systems	795
26-1	Generation of Three-Phase Voltages	796
26-2	Y-Connected Generator	798
	Phase Voltages and Currents	798
	Double Subscript Notation	799
	Line Currents and Voltages	799
	Y-Connected Loads	801
26-3	Delta-Connected Generator	805
	Voltages and Currents	805
	Delta-Connected Loads	808
26-4	Y- Δ and Y-Y Systems	813
	Y- Δ System	813
	Y-Y System	817
26-5	Phase Sequence	820
	Correct Phase Sequence	820
	Reversed Phase Sequence	820
	Phase Sequence Effects	822
	Phase Sequence Tester	823
26-6	Power in Three-Phase Systems	824
	True Power	824
	Reactive Power	825
	Apparent Power	825
26-7	Power Factor Correction	827
26-8	Three-Phase Power Measurement	830
	Wattmeter Use	830
	Three-Wattmeter Methods	830
	Single-Wattmeter Method	831
	Two-Wattmeter Method	832
	Power Factor Determination	835
Chapter 27	Non-Sinusoidal Waveforms	845
27-1	Miscellaneous Waveforms	845
27-2	Harmonics in Waveforms	847
	Frequency Synthesis and Harmonic Analysis	847
	Generation of Nonsinusoidal Waveforms	849
27-3	Harmonic Analysis	850
	Square Wave	850
	Sawtooth Wave	851
	Rectified Wave	852
	Amplitudes of Harmonics	852
27-4	RMS Value of Nonsinusoidal Waveforms	855
27-5	Nonsinusoidal Voltage as a Circuit Input	857
Chapter 28	Network Parameters	865
28-1	Impedance Parameters (z-Parameters)	866
	Open-circuit input and output impedances	866
	Open-Circuit Transfer Impedances	867

Impedance Summary	869
z -Parameter Equations	870
Equivalent Circuits	871
28-2 Admittance Parameters (y -Parameters)	874
Short-Circuit Admittance Parameters	874
Short-circuit Input and Output Admittances	874
Short-circuit Transfer Admittances	875
Parameter Summary	876
y -Parameter Equations	878
Equivalent Circuits	878
28-3 Hybrid Parameters (h -Parameters)	881
h -Parameter Equivalent Circuit	881
Parameter Definitions	881
Parameter Summary	883
Loaded Network	883
Current Gain (A_i)	883
Voltage Gain (A_v)	883
Input Impedance (Z_i)	884
Output Impedance (Z_o)	884
h -Parameter Approximations	885
28-4 Transmission Parameters (T -Parameters)	887
T -Parameter Equations	887
Parameter Definitions	888
Parameter Summary	890
28-5 Parameters Relationships	891
Chapter 29 Circuit Analysis by Computer	900
29-1 Series Resistor Circuit	901
Drawing the Circuit Using Micro-Cap (MC9)	901
Analysis Using Micro-Cap	902
Multisim	902
PSpice	904
29-2 Series-Parallel Resistor Circuits	904
Micro-Cap	904
Multisim	905
PSpice	906
29-3 DC Network Analysis	906
Micro-Cap	906
Multisim	907
PSpice	908
29-4 Circuit with a Variable Load Resistor	908
29-5 Transient Analysis	910
29-6 AC Network Analysis	911
29-7 Resonant Circuit Analysis	913
29-8 Filter Frequency Response	915

Chapter 30	Network Topology	923
30-1	Graph Theory	924
30-2	Branch Nodal Analysis	925
30-3	Link Loop Analysis	927
30-4	Tie-Set and Cut-Set Matrices	930
	Tie-set Matrix	930
	Cut-set Matrix	933
Chapter 31	Introduction to Laplace Transforms	937
31-1	Laplace Transform Basics	937
	Laplace Transform and Inverse Laplace Transform	937
	Laplace Transform Pair	938
	Complex Frequency	940
31-2	Determining Laplace Transforms	940
	Step Function	940
	Ramp function	940
	Exponential Function	940
	Impulse	941
	Sum of Functions	941
31-3	Determining Inverse Laplace Transforms	942
	Using the Table	942
	Fractions	943
	The Initial and Final Value Theorems	944
31-4	Laplace Transform Applications	946
	RL Circuit Analysis	946
	RC Circuit Analysis	948
Appendices		
Appendix 1	Circuit Symbols	955
Appendix 2	The International System of Units (SI Units)	956
Appendix 3	Unit Conversion Factors	962
Appendix 4	American Wire Gauge Sizes and Metric Equivalents	965
Appendix 5	Resistor Color Code	966
Appendix 6	Resistor and Capacitor Values	967
Appendix 7	Determinants	969
Appendix 8	Answers to Odd-Numbered Problems	977
Index		985

CHAPTER 1

Basics of Electricity

Objectives

You will be able to:

- 1 Explain electrification by friction and the concept of positive and negative electricity.
- 2 State the fundamental law of electrification by friction.
- 3 Describe the planetary atom and sketch a diagram to represent an atom and its component parts.
- 4 Describe what happens when an electric current flows.
- 5 Define a conductor, an insulator, and a resistance.
- 6 Explain potential difference and its relationship to current and resistance.
- 7 Sketch the basic construction of a voltage cell and discuss its operation.
- 8 Sketch the graphic symbols used to represent basic circuit components and draw simple circuit diagrams.
- 9 Explain conventional current direction and electron flow.
- 10 Explain the difference between direct current (dc) and alternating current (ac).
- 11 Discuss how electric shock occurs, and describe some of the situations in which electricity can be hazardous to humans.

INTRODUCTION

Human knowledge of electricity began with the study of the phenomenon known to experimenters as *electrification by friction*. The early concept of an electric fluid being transferred from one body to another is now understood as a motion of electrons that have become detached from their atoms. A flow of electrons constitutes an electric current, and the pressure that produces the electron flow is a potential difference between two bodies or between two terminals. A potential difference is produced by an excess of electrons on one body and/or a deficiency of electrons on the other. In the simplest source of electricity the excess and deficiency of electrons are the result of chemical action. When an electric current flows, heat is generated by the electron motion. In certain circumstances, light may also be produced—hence the electric lamp. The various components and interconnections of an electrical system comprise an electric circuit, and a circuit diagram is a graphic representation of an electric circuit. Because electricity can be dangerous, it is

important to use it carefully and to take immediate action when someone suffers an electric shock.

1-1 ELECTRIFICATION BY FRICTION

The study of electricity began with investigations of *electrification by friction*. The ancient Greeks knew that when amber was rubbed with wool it could attract lightweight particles of other material, such as feathers or lint. The Greek word *elektron*, which means amber, is the origin of the word *electricity*.

Early in the seventeenth century it was discovered that amber was not the only material that had this property. Glass rubbed with silk and ebonite rubbed with fur were both found capable of attracting small particles of other materials. It was also discovered that when two silk-rubbed glass rods were brought close together they were repelled from each other [see Figure 1-1(a)]. Also, when a silk-rubbed glass rod and a fur-rubbed ebonite rod were brought close together there was a force of attraction between them [Figure 1-1(b)].

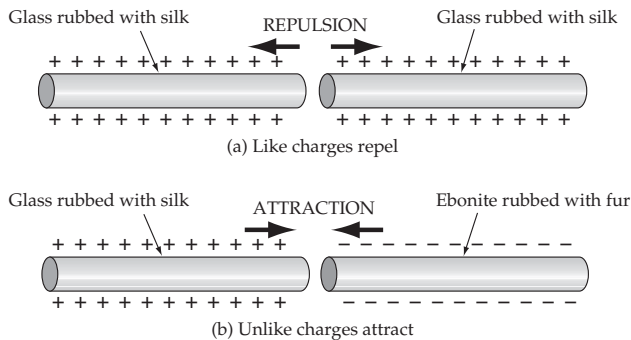


Figure 1-1 Glass and ebonite rods can be used to demonstrate electrification by friction. A silk-rubbed glass rod becomes positively charged. A fur-rubbed ebonite rod acquires a negative charge.

From these results it was concluded that there were two types of electricity and that materials *charged* with the same type of electricity repelled each other, while those charged with different types of electricity attracted each other. This conclusion produced a fundamental law:

Like charges repel; unlike charges attract.

Around the middle of the eighteenth century, Benjamin Franklin¹ suggested that when glass was rubbed with silk, some kind of *electric fluid* passed from the silk to the glass and that this gave the glass an increased

¹American statesman and scientist (1706–1790).

amount of electric fluid, or *positive charge*. Conversely, when ebonite was rubbed with fur, the electric fluid passed from the ebonite to the fur, he argued. Thus, the ebonite acquired a reduced amount of electricity, or *negative charge*.

The modern explanation of electrification by friction utilizes our present day understanding that the atom consists of a central *nucleus* surrounded by orbiting *electrons*. The diagram in Figure 1-2(a) illustrates the concept of the *planetary atom*. The electrons have a negative charge, and relative to the nucleus they are extremely small particles. The nucleus [Figure 1-2(b)] is largely a cluster of two types of particles, *protons* and *neutrons*, each of which has a mass approximately *1800 times the mass of the electron*. Neutrons have no charge at all, and protons have a positive charge equal in magnitude to the negative charge on an electron. Consequently, the nucleus is positively charged. The three basic particles—*proton*, *neutron*, and *electron*—are similar from one atom to another. Differences between atoms are due to differing numbers and arrangements of the three particles. Different materials are made up of different types of atoms or combinations of several types of atoms.

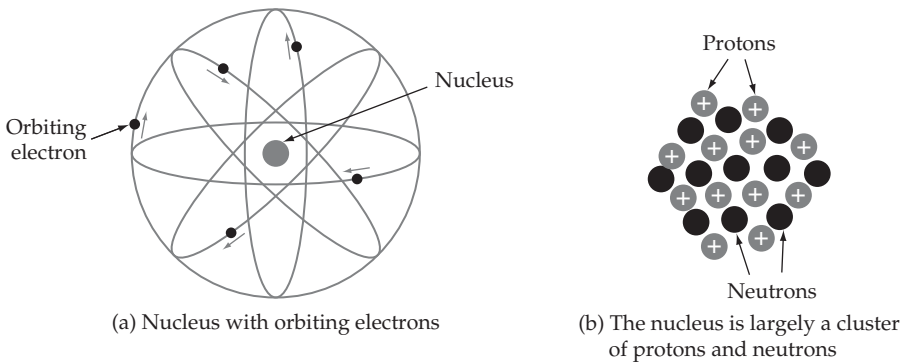


Figure 1-2 An atom consists of a central nucleus surrounded by orbiting electrons. The electrons have a negative charge and the protons in the nucleus have a positive charge.

It has been found that electrons can occupy only certain orbital rings, or *shells*, at fixed distances from the nucleus and that each shell can contain only a certain number of electrons. The outer shell is named the *valence shell*, and the electrons that occupy it are referred to as *valence electrons*. The valence electrons largely determine the electrical (and chemical) characteristics of an atom.

Because the protons and orbital electrons of an atom are equal in number and equal and opposite in charge, they neutralize each other electrically. So, each atom is normally electrically neutral; it exhibits neither a positive nor a negative charge. If an atom loses an electron it loses some negative charge,

and so it exhibits a positive charge. In this case the atom is referred to as a *positive ion*. Similarly, an atom that gains an additional electron becomes negatively charged and is then termed a *negative ion*.

Benjamin Franklin's electric fluid can now be looked upon as being composed of electrons passing from one material to another. The material that loses electrons becomes positively charged as the result of the loss of negative charges. The material that gains electrons becomes negatively charged. So, glass rubbed with silk acquires its positive charge by losing some electrons to the silk, and ebonite rubbed with fur becomes negatively charged by gaining electrons from the fur.

1-2 VOLTAGE, CURRENT, AND RESISTANCE

When two oppositely charged bodies make contact, electrons flow from the negatively charged body to the positively charged body. This means that electrons move from a location with an excess of electrons to one with a deficiency of electrons. Electrons will also flow from a negatively charged body to an uncharged body or to one with a lower negative charge.

The movement of electrons constitutes a flow of electric current.

The flow of charge carriers (i.e., electrons) also occurs if the two charged bodies are connected by a piece of metallic material (Figure 1-3). The flow does not occur when nonmetallic material is employed.

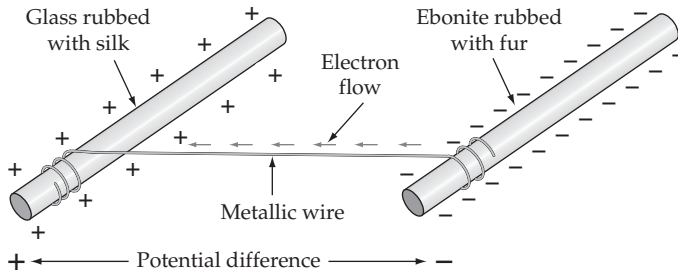


Figure 1-3 A potential difference (PD) exists between a negatively charged body and a positively charged body. When connected by a metallic wire, electrons flow from the negatively charged body to the positively charged body.

Materials that readily allow electrons to pass through them are termed conductors.

Materials that do not permit electron flow are known as insulators.

Because some materials are better conductors than others, it can be said that *they offer lower resistance to the flow of electric current*. Conductors obviously have much lower resistance than insulators. Electric current is measured in *amperes*, or *amps* (symbol A), and resistance is measured in *ohms* (symbol Ω —Greek letter omega).

The ability of two oppositely charged bodies to produce a flow of electricity between them may be thought of as a *potential* for the production of electric current. A positively charged body is said to have a *positive potential*, and a plus sign (+) is used to identify this potential on all diagrams. Similarly, a negatively charged body is described as having a *negative potential*, and a minus sign (−) is used for its identification. Two oppositely charged bodies are said to have a *potential difference* (PD) between them (see Figure 1-3). It is also possible for a potential difference to exist between two similarly charged bodies if one is charged to a higher potential than the other. Potential difference is measured in *volts* (symbol V), and the term *voltage* is commonly applied for potential difference. Another, more descriptive term for potential difference is *electromotive force* (emf).

Electromotive force is an electrical pressure that tends to cause current to flow when a suitable conducting path is provided.


Figure 1-4 compares the basic electrical quantities to the quantities in a water system. Water tank A in Figure 1-4(a) has a larger quantity of liquid than tank B. So, at the level of the connecting pipes, there is a pressure causing water to flow from tank A to tank B. Similarly, in Figure 1-4(b) body A has a larger quantity of electrons than body B. Consequently, there is an electrical pressure (electromotive force) causing a current of electrons to flow along the conductors from A to B. The large-diameter water pipe passes a greater water current than the small-diameter pipe, and the conductor with the large cross-sectional area passes a greater electrical current than the conductor with the small cross-sectional area. The large-diameter conductor offers less *resistance* to current flow than the small-diameter conductor.

Summarizing:


Voltage (emf, potential difference) is an electrical pressure that produces current flow (a movement of electrons) through a conductor.
Resistance is opposition to current flow.

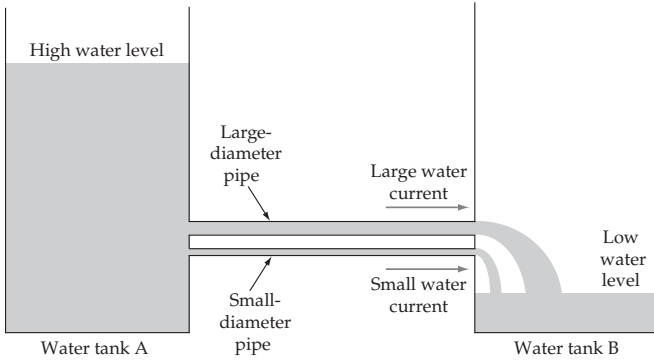1-3 BASIC SOURCE OF ELECTRICITY

The simplest modern source of electricity is a *zinc-carbon voltage cell*. As illustrated in Figure 1-5, the cell consists basically of a zinc can containing certain chemicals and having a centrally located carbon rod (see Chapter 10).



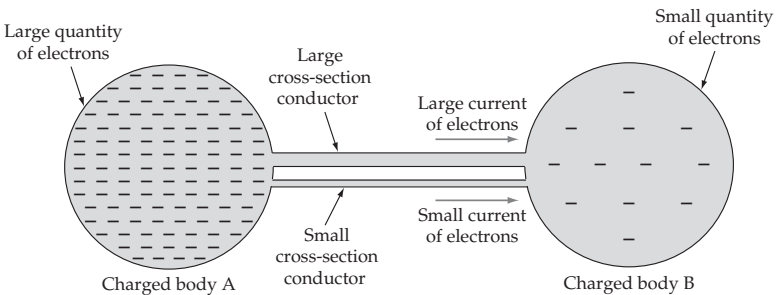(a) Water pressure causes a current of water to flow between two tanks. The large-diameter pipe passes a larger current of water than the small-diameter pipe.



(b) Electrical pressure (potential difference) causes a current of electrons to flow. The large cross-section conductor passes a greater electrical current than the small cross-section conductor. The large cross-section conductor has a *lower resistance* than the small cross-section conductor.

Figure 1-4 Comparison of water system and electrical system. In both systems a pressure difference causes a current to flow along a suitable path.

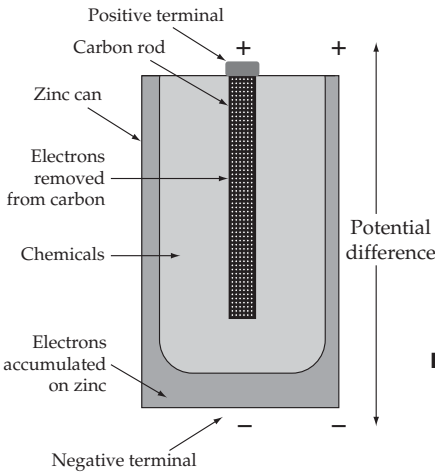


Figure 1-5 Cross-section of a zinc-carbon cell. Chemical action transfers electrons from the carbon to the zinc. The carbon rod is the positive terminal of the cell and the zinc can is the negative terminal.

Chemical action removes electrons from the carbon and causes them to accumulate on the zinc. Because the carbon has lost (negatively charged) electrons, it is positively charged. Also, the electron accumulation on the zinc makes the zinc negatively charged. The carbon rod is the *positive terminal* of the cell and the zinc can is the *negative terminal*. The outside of the zinc can is usually insulated and the bottom is left uncovered for connection purposes. A potential difference, or voltage, exists between the cell positive and negative terminals. When the terminals are connected via a suitable conducting path, electrons flow from the negative terminal to the positive.

1-4 ELECTRIC LAMP

Figure 1-6(a) illustrates the movement of electrons in a conductor when a potential difference is applied across the ends of the conductor. The electrons are repelled from the negative terminal and attracted toward the positive terminal. However, the atoms within the conductor impede the motion of the electrons, so that they cannot simply accelerate from the negative end to the positive end. Instead, each electron bounces about from one atom to another and merely drifts toward the positive end. Each time the electron strikes an atom, it dissipates energy in the form of heat. When a great many electrons are involved in a flow of current, the heat dissipation can be considerable. A simple electric lamp consists of a thin tungsten wire, or *filament*, contained in a glass bulb from which the air has been evacuated [see Figure 1-6(b)]. When a current of electrons is passed through the filament, many electron-atom collisions occur, and the resulting heat makes the filament glow white hot, so that it emits light.

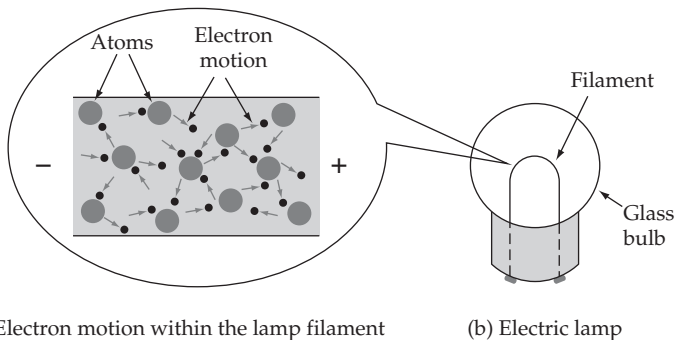


Figure 1-6 When a current of electrons flows in the filament of an electric lamp a great many electron-atom collisions occur. These collisions produce sufficient heat to cause the filament to glow.

1-5 ELECTRIC CIRCUIT

The flashlight circuit shown in Figure 1-7 is made up of a voltage cell, a switch, an electric lamp (or bulb), and connecting conductors. The voltage cell and lamp have already been discussed. In this case, the conductors are the spring at the bottom of the voltage cell, the metal tube that contains the cell, and the metal reflector which is connected to one terminal of the lamp. The switch is simply a thin sliding metal strip that can make or break contact between the tube/container and the reflector.

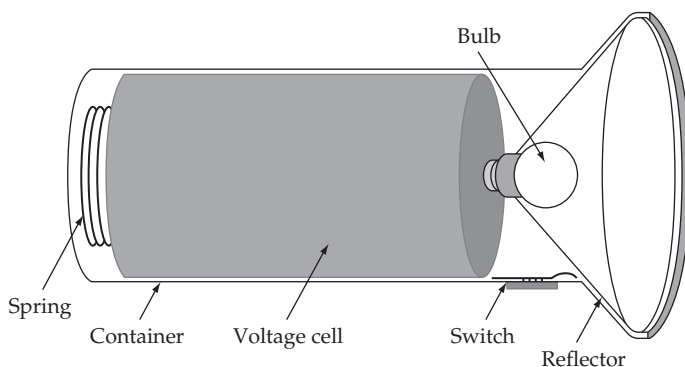


Figure 1-7 A flashlight consists of a battery, a light bulb, a switch, and connecting conductors.

Recall from Section 1-2 that a potential difference (voltage or emf) is an electrical pressure that causes current to flow when a suitable conducting path is provided. When the flashlight switch is open, the conducting path is interrupted so that no current flows. When the switch is closed, the potential difference between the terminals of the voltage cell causes a current of electrons to flow from the negative terminal through the conductors, the lamp filament, and the switch to the positive terminal of the cell.

The circuit in Figure 1-7 can be represented by a *circuit diagram* consisting of lines and graphic symbols. Figure 1-8(a) shows that a conductor is depicted by a straight line, and that the graphic symbol for a voltage cell is a long bar and a short bar side by side. The long bar represents the positive terminal and the short bar is the negative terminal. Lamp and switch symbols are also shown, and a *resistor* circuit symbol is illustrated. As will be explained later, a resistor is a component constructed to have a particular resistance value. Other circuit symbols are given in Appendix 1.

Figure 1-8(b) shows the complete diagram for the flashlight circuit in Figure 1-7. As illustrated on the diagram, the letter E is used to represent voltage (sometimes V is used instead of E), the letter I represents current, and R is used for resistance.

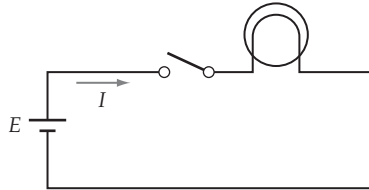
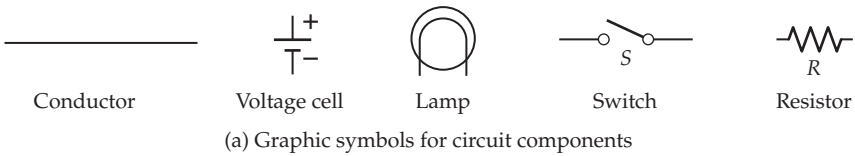


Figure 1-8 An electric circuit can be represented by a circuit diagram that uses graphic symbols for each component. The letter symbols E , I , and R identify voltage, current, and resistance respectively.

1-6 CURRENT DIRECTION

Early electrical researchers believed that a positive charge identified an increased quantity of electricity, and that a negative charge showed a reduced quantity. Consequently, they assumed that current flowed from positive to negative. This is a convention that remains in use today, even though current flow has long been accepted as a movement of electrons from negative to positive [see Figure 1-9(a)].

Current flow from positive to negative is known as the conventional current direction.

Electron flow from negative to positive is termed the direction of electron flow.

It is important to understand and to be able to think in terms of both conventional current direction and electron flow. Electron flow is used to explain how electronic devices operate, but *the graphic symbol for every electronic device employs an arrowhead that points in the direction of conventional current*. Figure 1-9(b) shows the symbol for the simplest electronic device; a *diode*. A diode is a one-way device; current flow occurs only when the polarity of the applied voltage is such that the arrowhead points from positive to negative. When the voltage is reversed (arrowhead pointing from negative to positive) current cannot flow. So, the arrowhead indicates the direction of *conventional current* flow.

Electronic component and equipment manufacturers normally use conventional current direction when they indicate current on a circuit diagram. Conventional current direction is employed throughout this book.

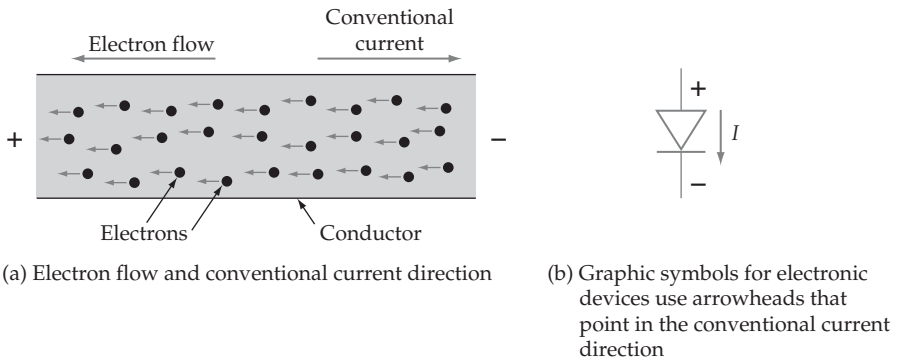


Figure 1-9 Electric current is a movement of electrons from negative to positive. Conventional current direction assumes current flow from positive to negative. All graphic symbols for electronic devices have arrowheads that indicate conventional current direction.

It should be noted that some books use the direction of electron motion as current direction.

1-7 DIRECT CURRENT AND ALTERNATING CURRENT

Current that flows continuously in one direction is termed *direct current* (abbreviated to dc). This is the kind of current supplied by a voltage cell. Because the voltage at the terminals of a voltage cell remains substantially constant, the current in a circuit supplied by the voltage cell also remains constant. A voltage cell can be described as a *direct voltage source*. Figure 1-10(a) shows the graph of direct current (I) plotted versus time (t); obviously, the current remains constant. The graphic symbol for a direct voltage source is also shown, and this is the voltage cell symbol already discussed.

Alternating current (abbreviated to ac) is current that flows first in one direction for a time (usually a fraction of a second), and then reverses to flow in the opposite direction for a similar time. This is illustrated in Figure 1-10(b), where a graph of alternating current (i) is plotted versus time (t). Note that the current level increases from zero to a peak (positive or negative) value, decreases to zero again, and then increases once more in the opposite direction. This cycle repeats over and over again. The circuit symbol for an alternating voltage source is also illustrated.

1-8 ELECTRIC SHOCK

Electricity can kill, and so it is very important to treat electrical supplies and equipment with great care. The greatest domestic danger exists in bathrooms and kitchens, because of the presence of water and water taps. Water pipes are connected to other pipes that are buried in the ground, so they provide an

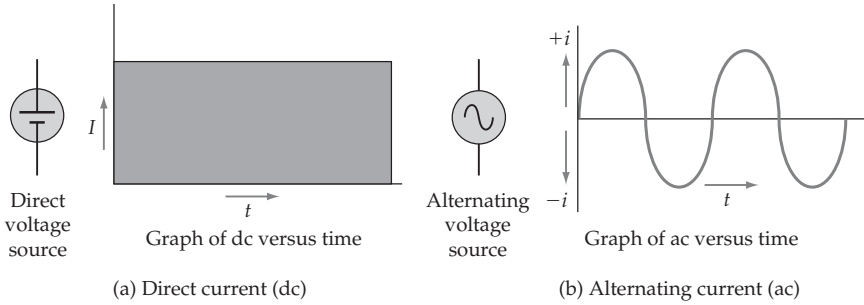


Figure 1-10 A graph of direct current (dc) plotted versus time shows that the current remains constant. A graph of alternating current (ac) versus time shows that the current repeatedly reverses, alternately flowing in one direction and then in the other.

electrical connection to ground. Normally, there is a high potential difference between at least one of the electric supply conductors and ground. Consequently, when a person holds a faulty appliance in one hand and a grounded water tap in the other, a path is provided for current to flow from the conductor to ground via the person. In this case the individual can experience a severe electric shock and may find it impossible to open either hand!

A similar danger exists when someone is using a portable appliance, such as an electric drill, if, for example, the supply cable is worn or has temporary taped splices. While holding the appliance in one hand and pulling the cable, the other hand might close around a bare wire. Here again it may be impossible to open either hand as the electricity flows through the body. An even more lethal situation exists when someone taking a bath reaches for an electrical appliance. The person's body is grounded via the water, and if the appliance is faulty *death is virtually inevitable*.

In a case of electric shock, it is most important to immediately get the victim away from the source of the shock. To avoid endangering a rescuer, the electricity supply must be switched off or disconnected before the victim is touched. Medical help should be summoned, and the victim should be made comfortable and kept calm. If the victim has stopped breathing, artificial respiration should be commenced and continued until medical help arrives. If the victim's heart has stopped beating, external heart compression should be applied by a trained individual.

Summary of Important Terms

- ◆ *Potential difference* (PD), *voltage*, and *electromotive force* (emf) are all names for the electrical pressure that tends to cause current flow.

- ◆ *Electrical current* is a movement of electrons from a negative potential to a positive potential.
- ◆ *Electrical resistance* is opposition to current flow.
- ◆ *Conventional current direction* is from positive to negative.
- ◆ *Electron flow* is electron movement from negative to positive.
- ◆ *Direct current* (dc) is current that constantly flows in a single direction.
- ◆ *Alternating current* (ac) is current that alternately flows in one direction and then in the opposite direction.

Review Questions

Section 1-1

- 1-1 Explain what is meant by electrification by friction. Also define positive and negative electricity as related to electrification by friction.
- 1-2 State the fundamental law that originated from the study of electrification by friction. Briefly explain the law.
- 1-3 Draw a diagram of the planetary atom. Identify the three basic particles that constitute an atom and define their relative quantities of charge and mass.
- 1-4 Define a valence electron and discuss the effect on an atom when it loses an electron and the effect when it gains an electron.

Section 1-2

- 1-5 Describe what occurs when an electric current flows between two charged bodies. Briefly define: conductor, insulator, resistance.
- 1-6 Explain what constitutes a potential difference and how it is related to electric current.

Section 1-3

- 1-7 Sketch the basic construction of a voltage cell and explain how it produces positive and negative terminals.

Section 1-4

- 1-8 Explain how electric current can produce light and briefly describe an electric lamp.

Section 1-5

- 1-9 Sketch a diagram for an electric circuit consisting of a voltage cell, a lamp, and a switch. Briefly explain the operation of the circuit.
- 1-10 Refer to the circuit symbols in Appendix 1. Sketch an electric circuit consisting of a generator, a switch, a resistor, and a lamp.

Section 1-6

- 1-11** Explain the difference between conventional current direction and direction of electron flow. Sketch the circuit diagram of a lamp supplied from a voltage cell, and identify the directions of conventional current flow and electron flow.
- 1-12** Sketch the circuit symbol for a diode showing the polarity of applied voltage for current flow. Show the direction of conventional current flow and the direction of electron movement.

Section 1-7

- 1-13** Define direct current, alternating current, emf, potential difference, and voltage.
- 1-14** Draw graphs to show the difference between direct current and alternating current. Briefly explain.

Section 1-8

- 1-15** Describe some of the most dangerous situations in which a person can suffer an electric shock. List the emergency actions that should be taken to aid a victim of electric shock.